

Diode Rectifiers and Filters

- In a half wave rectifier, the load current flows for what part of the cycle.
 - 0°
 - 90°
 - 180°
 - 360°
- In a full wave rectifier, the current in each diode flows for
 - whole cycle of the input signal
 - half cycle of the input signal
 - more than half cycle of the input signal
 - none of these
- In a full wave rectifier, if the input frequency is 50 Hz, then output frequency will be
 - 50 Hz
 - 75 Hz
 - 100 Hz
 - 200 Hz
- In a center tap full wave rectifier, if V_m is the peak voltage between center tap and one end of the secondary, the maximum voltage coming across the reverse bias diode is
 - V_m
 - $2 V_m$
 - $V_m/2$
 - $V_m/\sqrt{2}$
- The maximum efficiency of full wave rectification is
 - 40.6%
 - 100%
 - 81.2%
 - 85.6%
- In a bridge type full wave rectifier, if V_m is the peak voltage across the secondary of the transformer, the maximum voltage coming across each reverse biased diode is
 - V_m
 - $2 V_m$
 - $V_m/2$
 - $V_m/\sqrt{2}$
- To get a peak load voltage of 40V out of a bridge rectifier. What is the approximate rms value of secondary voltage?
 - 0 V
 - 14.4 V
 - 28.3 V
 - 56.6 V

8. If the line frequency is 50 Hz, the output frequency of bridge rectifier is
- a. 25 Hz
 - b. 50 Hz
 - c. 100 Hz
 - d. 200 Hz
9. The ripple factor of a bridge rectifier is
- a. 0.482
 - b. 0.812
 - c. 1.11
 - d. 1.21
10. The bridge rectifier is preferred to an ordinary two diode full wave rectifier because
- a. it needs much smaller transformer for the same output
 - b. no center tap required
 - c. less PIV rating per diode
 - d. all the above
11. The basic purpose of filter is to
- a. minimize variations in ac input signal
 - b. suppress harmonics in rectified output
 - c. remove ripples from the rectified output
 - d. stabilize dc output voltage
12. The use of a capacitor filter in a rectifier circuit gives satisfactory performance only when the load
- a. current is high
 - b. current is low
 - c. voltage is high
 - d. voltage is low
13. A half wave rectifier is equivalent to
- a. clamper circuit
 - b. a clipper circuit
 - c. a clamper circuit with negative bias
 - d. a clamper circuit with positive bias
14. The basic reason why a full wave rectifier has a twice the efficiency of a half wave rectifier is that
- a. it makes use of transformer
 - b. its ripple factor is much less
 - c. it utilizes both half-cycle of the input
 - d. its output frequency is double the line frequency

15. In a rectifier, larger the value of shunt capacitor filter
- a. larger the peak-to-peak value of ripple voltage
 - b. larger the peak current in the rectifying diode
 - c. longer the time that current pulse flows through the diode
 - d. smaller the dc voltage across the load
16. In a LC filter, the ripple factor,
- a. Increases with the load current
 - b. increases with the load resistance
 - c. remains constant with the load current
 - d. has the lowest value
17. The main reason why a bleeder resistor is used in a dc power supply is that it
- a. keeps the supply ON
 - b. improves voltage regulation
 - c. improves filtering action
 - d. both (b) and (c)
18. Which rectifier requires four diodes?
- a. half-wave voltage doubler
 - b. full-wave voltage doubler
 - c. full-wave bridge circuit
 - d. voltage quadrupler
19. The dc output polarity from a half-wave rectifier can be reversed by reversing
- a. the diode
 - b. transformer primary
 - c. transformer secondary
 - d. both (b) and (c)

Answers

- | | | | |
|---------|---------|---------|---------|
| 1. (c) | 2. (b) | 3. (c) | 4. (b) |
| 5. (c) | 6. (a) | 7. (c) | 8. (c) |
| 9. (a) | 10. (d) | 11. (c) | 12. (b) |
| 13. (b) | 14. (c) | 15. (b) | 16. (c) |
| 17. (d) | 18. (c) | 19. (a) | |