

Operational Amplifiers (OP-AMPS)

1. The op amp can amplify
 - a. AC signals only
 - b. DC signals only
 - c. Both ac and dc signals
 - d. Neither ac not dc signals

2. The input offset current equals the
 - a. Difference between the two base currents
 - b. Average of the two base currents
 - c. Collector current divided by current gain
 - d. Difference between the two base-emitter voltages

3. When the two input terminals of a diff amp are grounded
 - a. The base currents are equal
 - b. The collector currents are equal
 - c. An output error voltage usually exists
 - d. The ac output voltage is zero

4. A common-mode signal is applied to
 - a. The non-inverting input
 - b. The inverting input
 - c. Both inputs
 - d. The top of the tail resistor

5. The common-mode voltage gain is
 - a. Smaller than the voltage gain
 - b. Equal to the voltage gain
 - c. Greater than the voltage gain
 - d. None of the above

6. The input stage of an op amp is usually a
 - a. Differential amp
 - b. Class B push-pull amplifier
 - c. CE amplifier
 - d. Swamped amplifier

7. The common-mode rejection ratio is
 - a. Very low
 - b. As high as possible
 - c. Equal to the voltage gain
 - d. Equal to the common-mode voltage gain

8. The typical input stage of an op amp has a
 - a. Single-ended input and single-ended output
 - b. Single-ended input and differential output
 - c. Differential input and single-ended output
 - d. Differential input and differential output

9. The input offset current is usually
- Less than the input bias current
 - Equal to zero
 - Less than the input offset voltage
 - Unimportant when a base resistor is used
10. With both bases grounded, the only offset that produces an error is the
- Input offset current
 - Input bias current
 - Input offset voltage
 - β
11. The voltage gain of a loaded differential amp is
- Large than the unloaded voltage gain
 - Equal to R_C / r_e
 - Smaller than the unloaded voltage gain
 - Impossible to determine
12. At the unity-gain frequency, the open-loop voltage gain is
- 1
 - $A_{V(\text{mid})}$
 - Zero
 - Very large
13. If the cutoff frequency is 20 Hz and the mid-band open-loop voltage gain is 1,000,000 the unity-gain frequency is
- 20 Hz
 - 1 MHz
 - 2 MHz
 - 20 MHz
14. When the initial slope of a sine wave is greater than the slew rate.
- Distortion occurs
 - Linear operation occurs
 - Voltage gain is maximum
 - The op amp works best
15. A 741 C contains
- Distortion resistors
 - Inductors
 - Active-load resistors
 - A large coupling capacitor
16. The input impedance of a BIFET op amp is
- Low
 - Medium
 - High
 - Extremely high
17. The 741 C has a unity-gain frequency of
- 10 Hz
 - 20 Hz
 - 1 MHz
 - 15 MHz

18. An op amp has a voltage gain of 200,000. If the output voltage is 1 V, the input voltage is
- | | |
|--------------|---------|
| a. 2 μ V | c. 10 V |
| b. 5 μ V | d. 1 V |
19. A 741 C has
- | | |
|---------------------------------------|---------------------------------------|
| a. A voltage gain of 100,000 | c. An output impedance of 75 Ω |
| b. An input impedance of 2 M Ω | d. All of the above |
20. The voltage follower has a
- Closed-loop voltage gain of unity
 - Small open-loop voltage gain
 - Closed-loop bandwidth of zero
 - Large closed-loop output impedance
21. An instrumentation amplifier has a high
- | | |
|---------------------|-------------------|
| a. Output impedance | c. CMRR |
| b. Power gain | d. Supply voltage |
22. In a differential amplifier, the CMRR is limited mostly by the
- | | |
|---------------------------|-------------------------------|
| a. CMRR of the op amp | c. Supply voltages |
| b. Gain-bandwidth product | d. Tolerance of the resistors |
23. The input signal for an instrumentation amplifier usually comes from
- | | |
|---------------------------|-----------------------------|
| a. An inverting amplifier | c. A differential amplifier |
| b. A resistor | d. A wheat- stone bridge |
24. In a nonlinear op-amp circuit, the
- Op amp never saturates
 - Feedback loop is never opened
 - Output shape is the same as the input shape
 - Op amp may saturate
25. To detect when the input is greater than a particular value, use a
- | | |
|---------------|---------------|
| a. Comparator | c. Limiter |
| b. Clamper | d. Relaxation |
26. The voltage out of a Schmitt trigger is
- | | |
|-------------------|-----------------------------------|
| a. A low voltage | c. Either a low or a high voltage |
| b. A high voltage | d. A sine wave |

27. Hysteresis prevents false triggering associated with
- a. A sinusoidal input
 - b. Noise voltages
 - c. Stray capacitances
 - d. Trip points
28. If the input is a rectangular pulse, the output of an integrator is a
- a. Sine wave
 - b. Square wave
 - c. Ramp
 - d. Rectangular pulse
29. When a large sine wave drives a Schmitt trigger, the output is a
- a. Rectangular wave
 - b. Triangular wave
 - c. Rectified sine wave
 - d. Series of ramps
30. A comparator with a trip point of zero is sometimes called a
- a. Threshold detector
 - b. Zero-crossing detector
 - c. Positive limit detector
 - d. Half-wave detector
31. A Schmitt trigger uses
- a. Positive feedback
 - b. Negative feedback
 - c. Compensating capacitors
 - d. Pull up resistors
32. A Schmitt trigger
- a. Is a zero-crossing detector
 - b. Has two trip points
 - c. Produces triangular output waves
 - d. Is designed to trigger on noise
33. The trip point of a comparator is the input voltage that causes
- a. The circuit to oscillate
 - b. Peak detection of the input signal
 - c. The output to switch states
 - d. Clamping to occur
34. An active half-wave rectifier has a knee voltage of
- a. V_K
 - b. 0.7 V
 - c. More than 0.7 V
 - d. Much less than 0.7 V
35. In an active peak detector, the discharging time constant is
- a. Much longer than the period
 - b. Much shorter than the period
 - c. Equal to the period
 - d. The same as the charging time constant

36. A window comparator
- a. Has only one usable threshold
 - b. Uses hysteresis to speed up response
 - c. Clamps the input positively
 - d. Detects an input voltage between two limits

Answers

- | | | | |
|---------|---------|---------|---------|
| 1. (c) | 2. (a) | 3. (c) | 4. (c) |
| 5. (a) | 6. (a) | 7. (b) | 8. (c) |
| 9. (a) | 10. (c) | 11. (c) | 12. (a) |
| 13. (d) | 14. (a) | 15. (c) | 16. (d) |
| 17. (c) | 18. (b) | 19. (d) | 20. (a) |
| 21. (c) | 22. (d) | 23. (d) | 24. (d) |
| 25. (a) | 26. (c) | 27. (b) | 28. (c) |
| 29. (a) | 30. (b) | 31. (a) | 32. (b) |
| 33. (c) | 34. (d) | 35. (a) | 36. (d) |

GATESTUDY.COM