

FET-AMPLIFIER

1. A field effect transistor (FET)
 - a. Uses a forward bias p-n junction
 - b. Uses a high concentration emitter junction
 - c. Has a very high input resistance
 - d. Depends on flow of minority carrier

2. As compared to transistor amplifier JFET amplifier has
 - a. Higher voltage gain, less input impedance
 - b. Less voltage gain, less input impedance
 - c. Less voltage gain, higher input impedance
 - d. Higher voltage gain, higher input impedance

3. The best location for setting a Q-point on dc load line of an FET Amplifier is at
 - a. Saturation point
 - b. Cutoff point
 - c. Mid- point
 - d. None of these

4. The pinch off voltage is the voltage
 - a. At which gate source junction breaks down
 - b. Which causes depletion regions to meet
 - c. The voltage applied between drain & source
 - d. Neither of these

5. If properly biased JFET acts as
 - a. Current controlled current source
 - b. Voltage controlled voltage source
 - c. Voltage controlled current source
 - d. Current controlled voltage source

6. The voltage gain of a common source JFET amplifier depends upon its
- Transconductance (g_m)
 - Amplification factor (μ)
 - External load resistance
 - Both (a) and (c)
7. A common gate amplifier has
- High input resistance and high output resistance
 - Low input resistance and high output resistance
 - Low input resistance and low output resistance
 - High input resistance and low output resistance
8. The transconductance g_m of JFET is equal to
- $-2 \cdot \frac{I_{DSS}}{V_P}$
 - $-2 \cdot \frac{I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$
 - $\frac{2}{|V_P|} \sqrt{I_{DSS} \cdot I_D}$
 - $\frac{I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$
9. A transconductance amplifier has
- High input impedance and low output impedance
 - Low input impedance and high output impedance
 - High input and output impedances
 - Low input and output impedances
10. A JFET is similar in operation to
- Diode
 - Pentode
 - Triode
 - Tetrode
11. In a common source JFET amplifier the output voltage is
- 180° out of phase with input
 - In phase with input
 - 90° out of phase with input
 - None of the above

12. A common source (CS) amplifier has a voltage gain of

- a. $g_m r_d$
- b. $g_m r_s$
- c. $g_m r_s / (1+g_m r_s)$
- d. $g_m r_d / (1+g_m r_d)$

13. A source follower has a voltage gain of

- a. $g_m r_d$
- b. $g_m r_s$
- c. $g_m r_s / (1+g_m r_s)$
- d. $g_m r_d / (1+g_m r_d)$

14. A cascode amplifier has the advantage of

- a. Large voltage gain
- b. Low input capacitance
- c. Low input impedance
- d. Higher g_m

15. If a JFET has $I_{DSS}=8\text{mA}$ and $V_P=4\text{V}$, then R_{DS} equals

- a. 200Ω
- b. 320Ω
- c. 500Ω
- d. $5\text{K}\Omega$

Answers

- 1. (c)
- 2. (c)
- 3. (c)
- 4. (b)
- 5. (c)
- 6. (d)
- 7. (b)
- 8. (b)
- 9. (a)
- 10. (b)
- 11. (a)
- 12. (a)
- 13. (c)
- 14. (b)
- 15. (c)