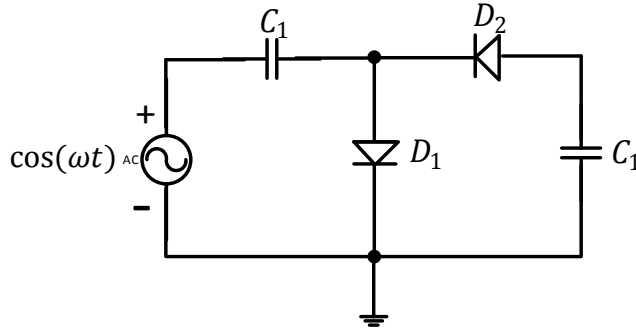


Diode Circuits – Recent GATE Problems

1. The diodes and capacitors in the circuit shown are ideal. The voltage $v(t)$ across the diode D_1 is



- (a) $\cos(\omega t) - 1$
 (b) $\sin(\omega t)$

- (c) $1 - \cos(\omega t)$
 (d) $1 - \sin(\omega t)$

[GATE 2012: 1 Mark]

Soln. Given,


Voltage $v(t) = \cos \omega t$

**Find the voltage across the diode D_1 (diodes and capacitors are ideal)
 When the positive cycle of the input is applied diode D_1 is forward biased and D_2 is reverse biased.**

Capacitor C_1 charges to maximum voltage (here 1 V)

When negative cycle of the input comes D_1 is reverse biased, so replaced by open.

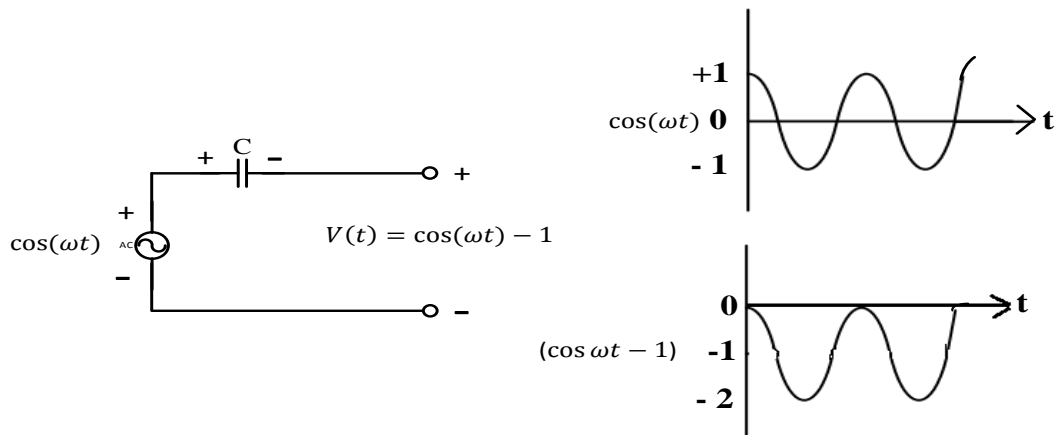Note that D_2 is reverse biased forever and can be replaced by a open switch.




In this circuit C_1 & D_1 form a clamper circuit while D_2 and C_2 form peak detector. This cascaded circuit acts as peak to peak detector.

Option (a)

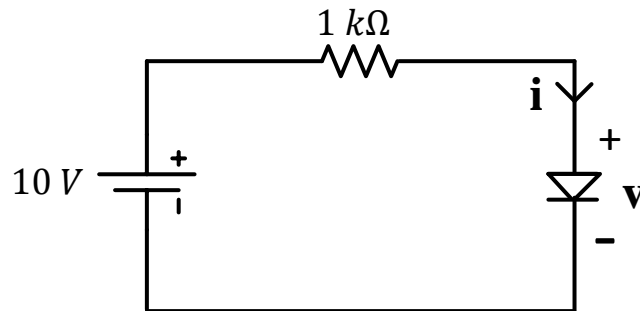2. The $i - v$ characteristics of the diode in the circuit given below are

$$i = \begin{cases} \frac{v - 0.7}{500} A, & v \geq 0.7 V \\ 0 A, & v < 0.7 V \end{cases}$$



The current in the circuit is


- (a) 10 mA
- (b) 9.3 mA
- (c) 6.67 mA
- (d) 6.2 mA

[GATE 2012: 1 Mark]

Soln. As per the given $i - v$ characteristics

$$i = \frac{v - 0.7}{500} A \text{ for } v \geq 0.7 V \text{ ----- (1)}$$
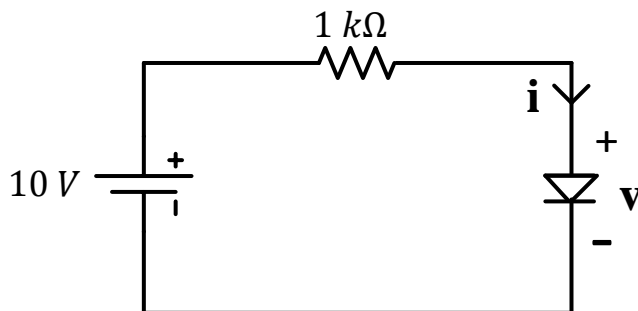
$$\text{From the given circuit, } v = 10 - 1000i \text{ ----- (2)}$$




From equation (1) and (2) eliminate v

$$i = \frac{10 - 1000i - 0.7}{500} = \frac{9.3}{500} - 2i$$

$$\text{or, } 3i = \frac{9.3}{500} \quad \text{or } i = \frac{3.1}{500} = 6.2\text{mA}$$

Thus, option (d)

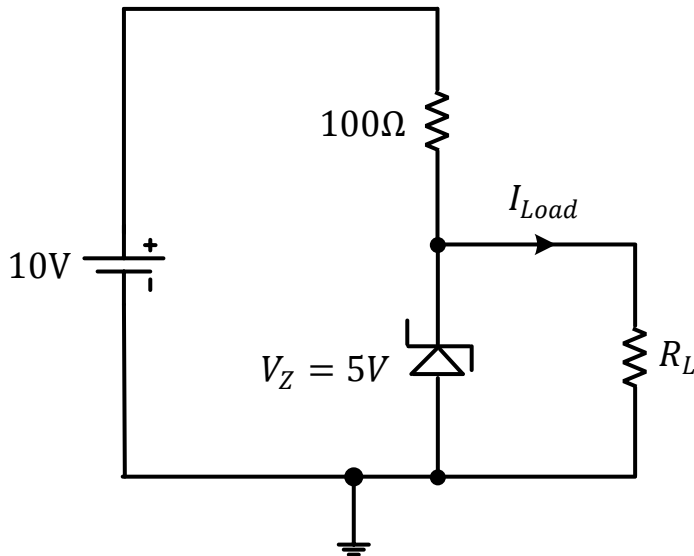3. In the circuit shown below, the knee current of the ideal Zener diode is 10 mA. To maintain 5 V across R_L , the minimum value of R_L in Ω and the minimum power rating of the Zener diode in mW, respectively are



- (a) 125 and 125
(b) 125 and 250

- (c) 250 and 125
(d) 250 and 250

[GATE 2013: 2 Marks]

Soln. Given,

Knee current of Zener (I_{zk}) = 10mA

Knee current of Zener is the minimum current that should flow through the diode for proper Zener action

Zener is of 5V i.e. $V_z = 5V$

Find, minimum R_L and diode power rating.

The minimum value of R_L means the load current is maximum (I_{max})

So,

$$V_{RL} = I_{Lmax} \cdot R_{min}$$

$$\text{or, } R_{min} = \frac{V_{RL}}{I_{Lmax}} = \frac{5}{I_{Lmax}} \quad \text{-----(1)}$$

Note,

$$I = I_{zk} + I_{Lmax}$$

$$\text{or, } I_{Lmax} = I - I_{zk} = 50 - 10 = 40mA$$

$$R_{min} = \frac{5}{40 \times 10^{-3}} = \frac{5000}{40} = \frac{500}{4} = 125\Omega$$


Minimum power rating of Zener diode.

It will be decided by the maximum current in Zener.

$$\begin{aligned} P_z &= V_z \cdot I_{zmax} \\ &= 5 \times 50 \text{ mA} = 250 \text{ mW} \end{aligned}$$

Option (b)

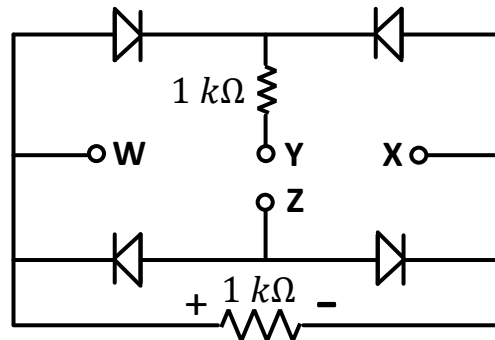4. A voltage $1000 \sin(\omega t)$ volts is applied across YZ. Assuming ideal diodes, the voltage measured across WX in volts, is



- (a) $\sin(\omega t)$ (c) $(\sin \omega t - |\sin \omega t|)/2$
 (b) $(\sin \omega t + |\sin \omega t|)/2$ (d) 0 for all t

[GATE 2013: 2 Marks]

Soln. Voltage applied across Y – Z terminals $v_i = 1000 \sin \omega t$

Diodes are assumed ideal

For positive cycle of the input

All four diodes are Reverse biased

$$V_W - V_X = 0$$

$$\text{or, } V_{WX} = 0$$

For negative cycle of the input

All diodes are forward biased i.e. short circuited


$$V_{WX} = V_W - V_X = 0$$

Thus,

V_{WX} is zero for all times

Option (d)

5. The figure shows a half-wave rectifier. The diode D is ideal. The average steady-state current (in Amperes) through the diode is approximately ____

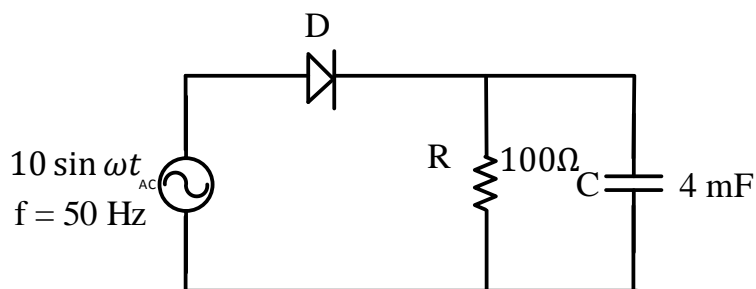

[GATE 2014: 1 Mark]

Soln. Given,

Input signal = $10 \sin \omega t$

Frequency = 50 Hz


Period of the waveform $T = \frac{1}{f} = \frac{1}{50} = 20 \text{ m sec}$

Time constant = $RC = 100 \times 4 \times 10^{-3} \text{ sec.}$
 $= 400 \text{ m sec.}$

Note here,

$$RC \gg T$$

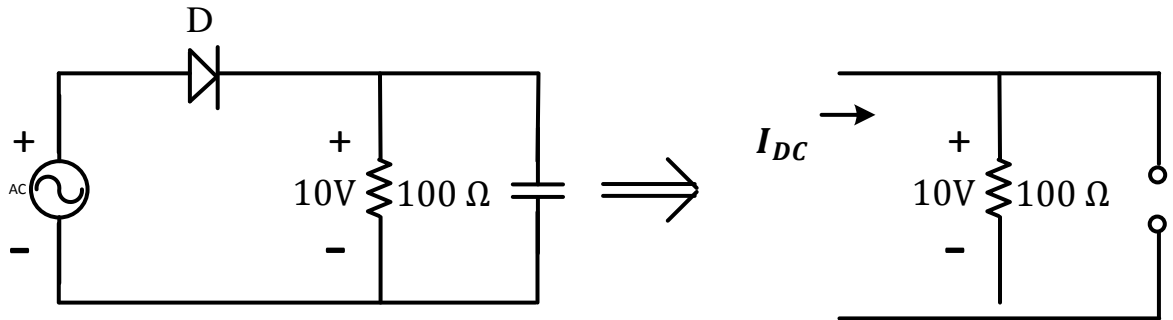Thus the voltage across the resistor can be approximated to 10V (DC).



Current through the diode


$$I_D(DC) = \frac{10V}{100} = 0.1 A$$

This circuit is also sometimes called half wave peak detector. In AM receives it is used to detect envelope of AM wave

Answer 0.1 A

6. Two silicon diodes, with a forward voltage drop of 0.7 V, are used in the circuit shown in the figure. The range of input voltage V_i for which the output voltage $V_0 = V_i$ is

- (a) $-0.3 V < V_i < 1.3 V$ (c) $-1.0 V < V_i < 2.0 V$
 (b) $-0.3 V < V_i < 2 V$ (d) $-1.7 V < V_i < 2.7 V$

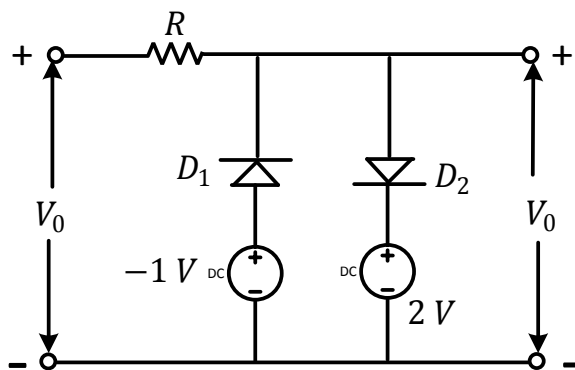

[GATE 2014: 1 Mark]

Soln. Given,

Forward voltage drop of the given Si diodes is 0.7V

Find, the range of V_i for which output voltage $V_0 = V_i$

Let us see the D_2 branch of the circuit.

D_2 will be forward biased when $V_i > 0.7 + 2 = 2.7V$

D_2 will be Reverse biased when $V_i < 2.7V$

See the branch D_1

D_1 will be forward biased when $V_i < -1 - 0.7 = 1.7V$

D_1 will be Reverse biased when $V_i > -1.7V$

When both the diodes will be Reverse biased (both shunt branches will be open) then $V_0 = V_{in}$

Thus, it will happen when

D_2 is Reverse biased i.e. $V_i < 2.7V$






D_1 is Reverse biased i.e. $V_i > -1.7V$

Thus,

$$-1.7V < V_i < 2.7V$$


Option (d)

7. For the circuit with ideal diodes shown in the figure, the shape of the output (V_{out}) for the given sine wave input (V_{in}) will be

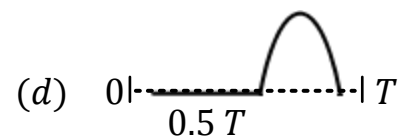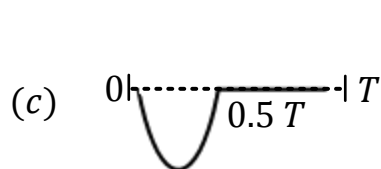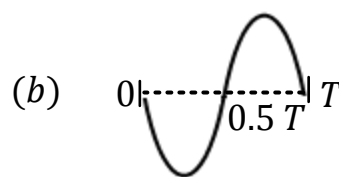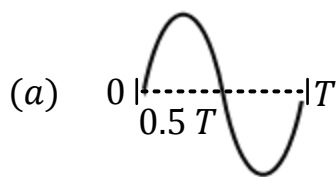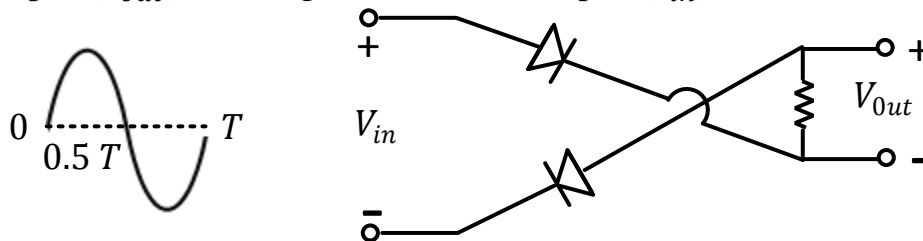

[GATE 2015: Mark]

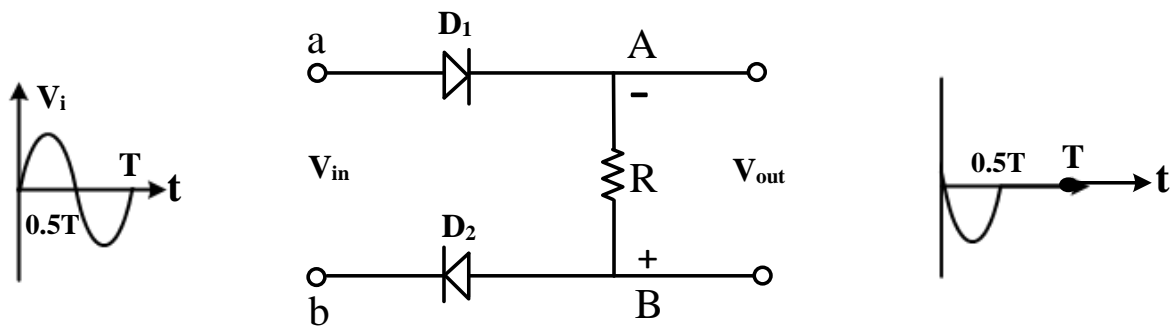Soln. The given circuit can be redrawn as



For +ve half cycle of the input

D_1 and D_2 are ON

$$V_{out} = -V_{in}$$


For -ve half cycle of the input

D_1 and D_2 are off

$$V_{out} = 0V$$

Option (c)

8. In the circuit shown below, the Zener diode is ideal and Zener voltage is 6 V. The output voltage V_0 (in volts) is _____.

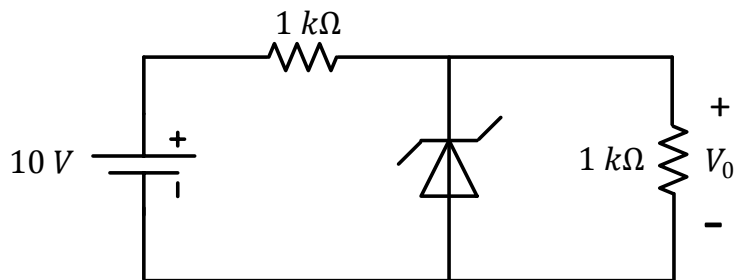

[GATE 2015: 1 Mark]

Soln. Given,

Zener voltage = 6 V


Zener diode is reverse biased during its operation. Here with the applied voltage, the voltage across the Zener diode is

$$V_0 = \frac{1\text{K}\Omega}{1\text{K} + 1\text{K}\Omega} \times 10V = 5V$$

Diode will be reverse biased but not in the Zener region, so open circuited.

Answer Thus, $V_0 = 5V$

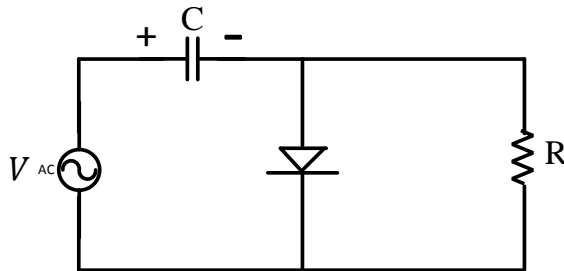9. If the circuit shown has to function as a clamping circuit, then which one of the following conditions should be satisfied for the sinusoidal signal of period T ?




- (a) $RC \ll T$
(b) $RC = 0.35 T$

- (c) $RC = T$
(d) $RC \gg T$

[GATE 2015: 1 Mark]

Soln. Observe the following circuit

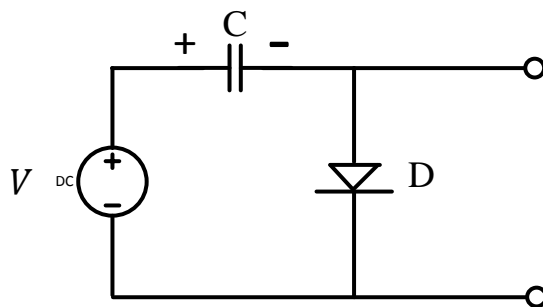

This circuit is of a negative clamper.

The present circuit has a load resistor connected in shunt.


When diode is off the capacitor discharges through resistor R . The output falls exponentially with time constant RC to avoid the discharge of capacitor significantly

$RC \gg T$

Where T is period of the sinusoidal waveform applied to the given circuit.

Option (d)

10. The diode in the circuit given below has $V_{ON} = 0.7 V$ but ideal otherwise. The current (in mA) in the $4 k\Omega$ resistor is _____.

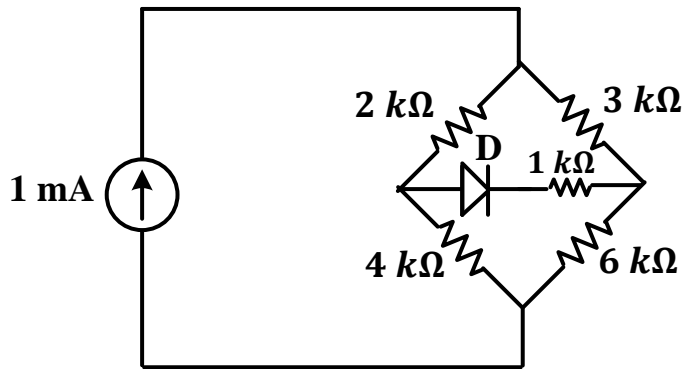

[GATE 2015: 2 Marks]

Soln. The given circuit is a bridge circuit note that the cross arm product is same i.e.

$$2 \times 6 = 4 \times 3$$

$$12 = 12$$

So, bridge is balanced

So no current through 1 kΩ resistor


Now current through 4 kΩ resistor will be

$$I = \frac{9}{9 + 6} \times 1 \text{ mA}$$

$$= \frac{9}{15} \text{ mA} = 0.6 \text{ mA}$$


Answer 0.6 mA

11. In the circuit shown, assume that diodes D_1 and D_2 are ideal. In the steady-state condition the average voltage V_{ab} (in Volts) across the $0.5 \mu\text{F}$ capacitor is _____.

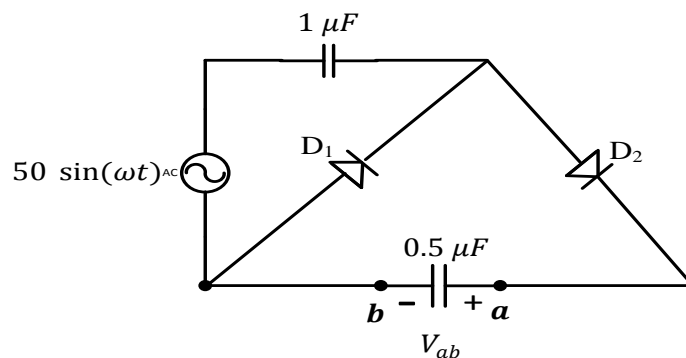

[GATE 2015: 1 Mark]

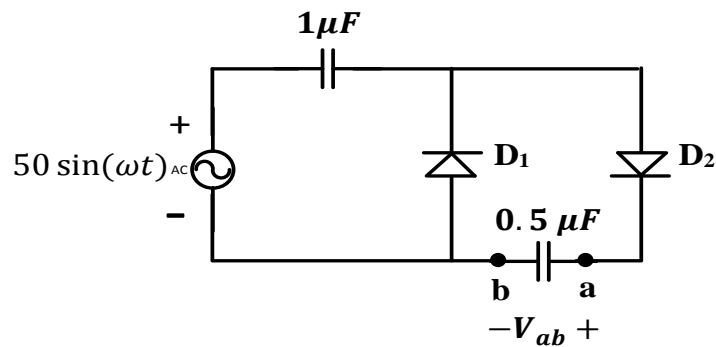Soln. The given circuit can be redrawn as follows:




During -ve half cycle of the applied sinewave input

D_1 is forward biased

Applying KVL

$$-50 + V_{C1} = 0$$

$$\text{or, } V_{C1} = 50V$$

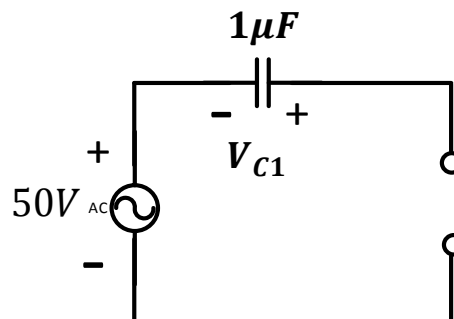


During +ve cycle of input

Applying KVL


$$50 + 50 - V_{ab} = 0$$

$$\text{or, } V_{ab} = 100V$$

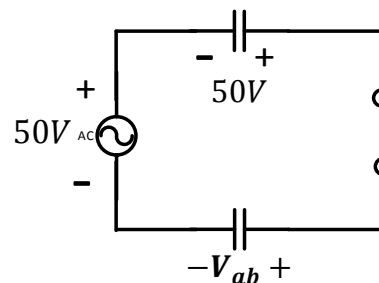

Answer 100V

12. In the circuit shown, assume that the diodes D_1 and D_2 are ideal. The average value of voltage V_{ab} (in volts) across terminals 'a' and 'b' is ____.

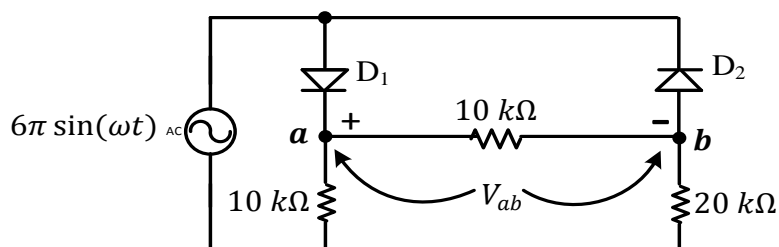


[GATE 2015: 1 Mark]

Soln. During positive cycle of the input

D₁ is Forward biased and

D₂ is Reverse biased

The circuit reduces to

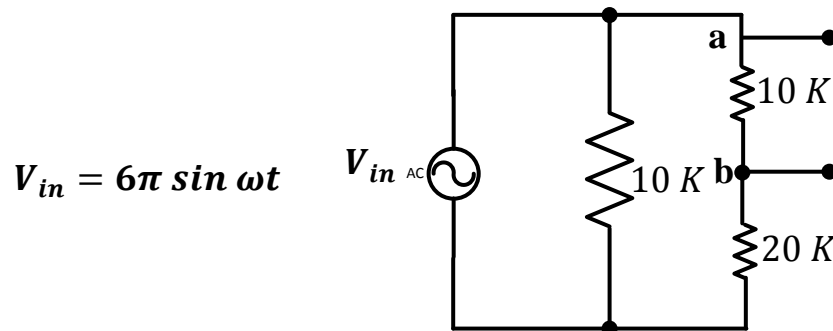

$$V_{ab} = \frac{10 K}{10 K + 20 K} \cdot V_{in}$$

$$= \frac{V_{in}}{3} = \frac{6\pi \sin \omega t}{3} = 2\pi \sin \omega t$$



During negative cycle of the input

D₁ is Reverse biased

D₂ is Forward biased

$$V_{ab} = \frac{10K}{10K + 10K} \cdot V_{in} = V_{in}/2$$

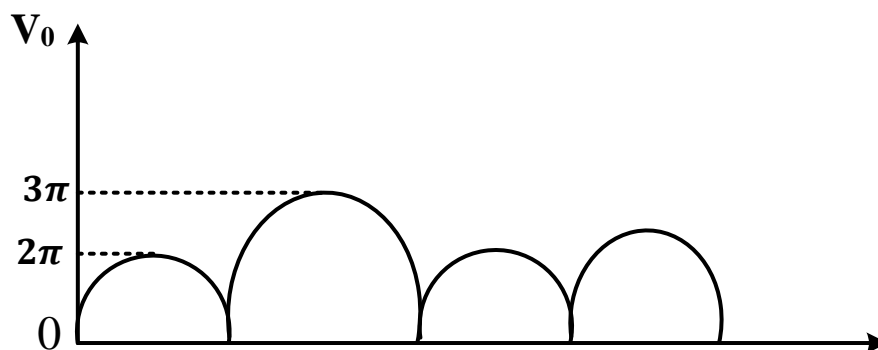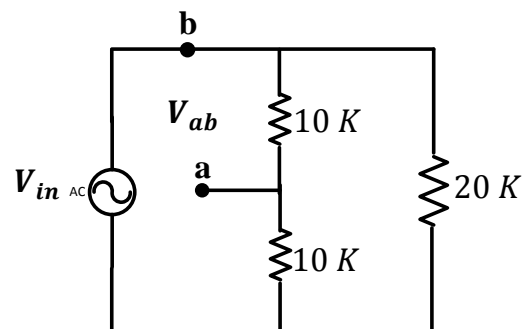
$$= \frac{6\pi \sin \omega t}{2} = 3\pi \sin \omega t$$



$$V_{ab} = \frac{2\pi}{\pi} + \frac{3\pi}{\pi} = 5 \text{ volts}$$

Answer: 5 volts

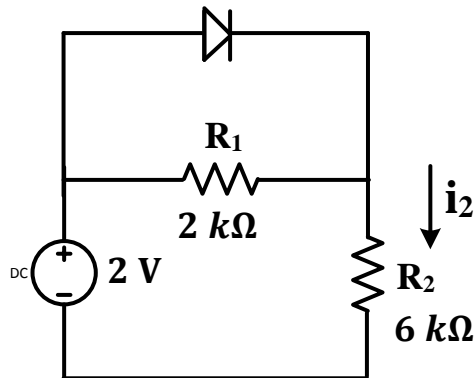
13. Assume that the diode in the figure has $V_{on} = 0.7 \text{ V}$, but is otherwise ideal.




The magnitude of the current i_2 (in mA) is equal to _____

[GATE 2016: 1 Mark]

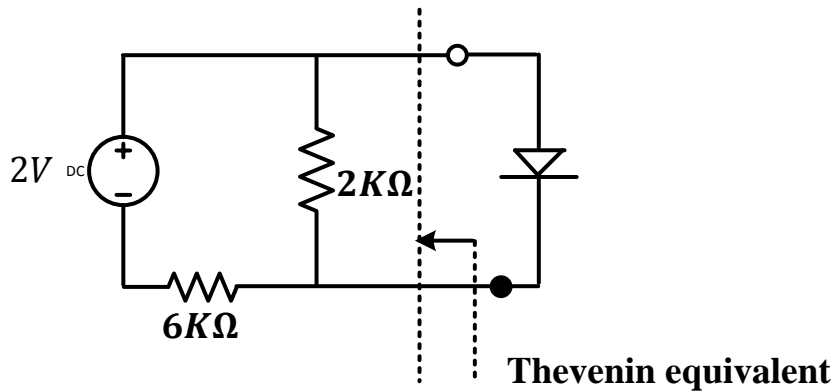
Soln. The given circuit can be redrawn as



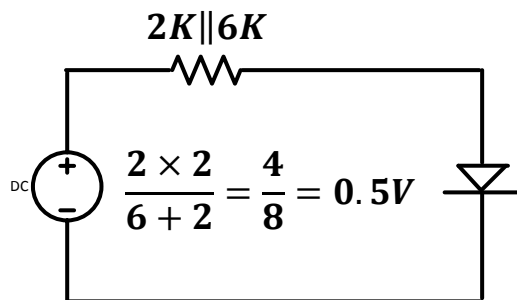This circuit can be further simplified using Thevenins theorem



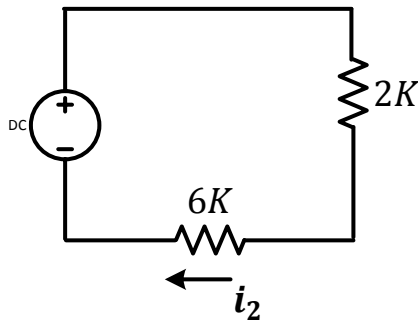Voltage across diode is 0.5V thus the diode is OFF. The circuit reduces to




The current through 6 K

$$i_2 = \frac{2}{2K + 6K} = \frac{2}{8K} = 0.25 \text{ mA}$$


Answer: 0.25 mA

14. The diodes D1 and D2 in the figure are ideal and the capacitors are identical. The product RC is very large compared to the time period of the ac voltage. Assuming that the diodes do not breakdown in the reverse bias, the output voltage V_0 (in volt) at the steady state is _____

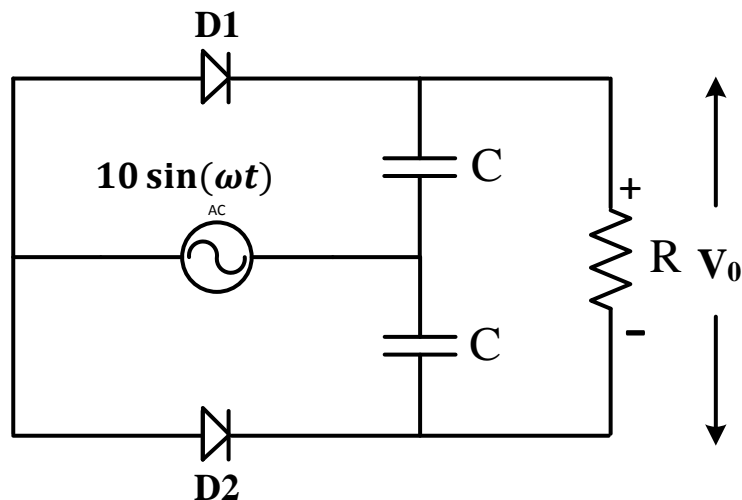

[GATE 2016: 1 Mark]

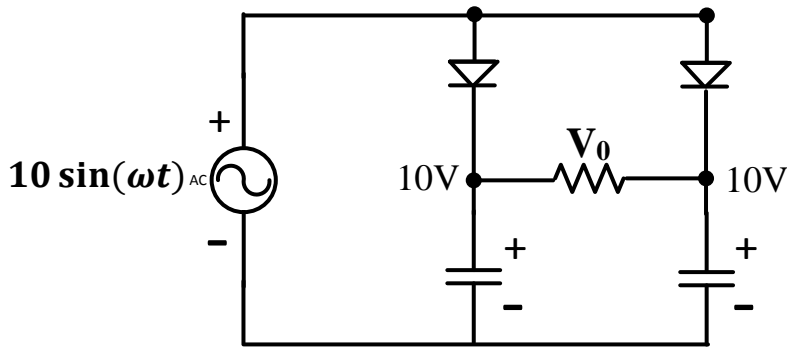Soln. Diodes D_1 and D_2 are ideal. The above circuit can be redrawn as




During positive cycle of input D_1 and D_2 are shorted thus $V_0 = 0V$

During negative cycle the diodes are reverse biased

$$V_0 = 0V$$

Thus $V_0 = 0V$ all the times

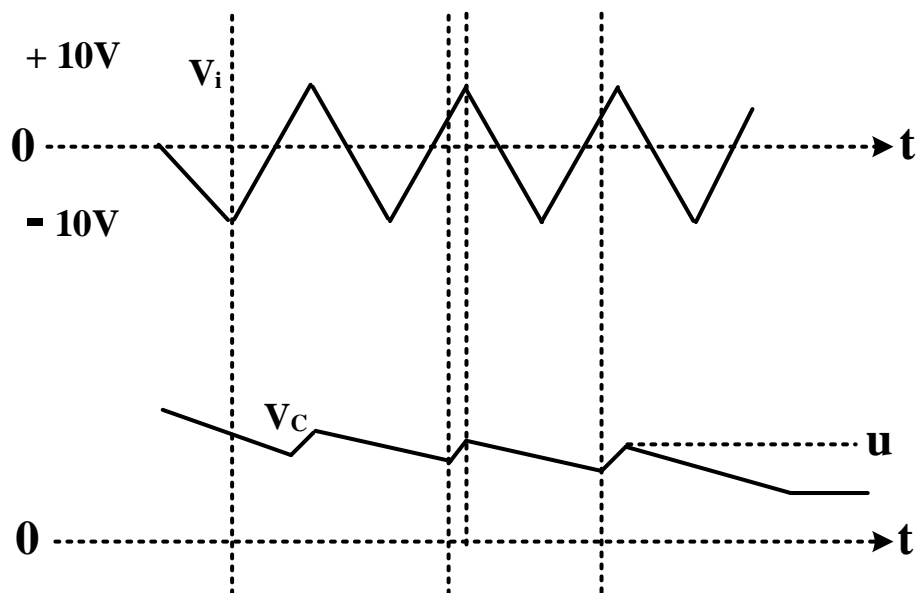15. The figure shows a half-wave rectifier with a $475 \mu\text{F}$ filter capacitor. The load a draws a constant current $I_0 = 1 \text{ A}$ from the rectifier. The figure also shows the input voltage V_i the output voltage V_c and the peak-to-peak voltage ripple u on V_c . The input voltage V_i is a triangle-wave with an amplitude of 10V and a period of 1 ms .



The value of the ripple u (in volts) is _____.

[GATE 2016: 2 Marks]

Soln. Given,

Half wave rectifier circuit

Filter capacitor = 475 μ F

Load draws constant current of 1 Amp.

The input voltage is triangular.

Output voltage V_c is given

One has to determine ripple (peak to peak)

Amount of charge lost by the capacitor should be equal to the charge gained during charging i.e

$$I_{dc} \cdot T = V_{r(p-p)} \cdot C$$

$$\begin{aligned} \text{Thus, } V_{r(p-p)} &= \frac{I_{dc} \cdot T}{C} = \frac{1A \cdot 1 \times 10^{-3}}{475 \times 10^{-6}} \\ &= \frac{1}{475} \times 10^3 = 2.1V \end{aligned}$$